

Student 1	
NAME	Zeyang Xu
ID	260923070
Student 2	
NAME	Kaicheng Wu
ID	260892789
Student 3 (if applicable)	
NAME	
ID	

Question 1 (1 mark)

Provide the VHDL code that you wrote for the wrapper circuit.

```

library IEEE;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use IEEE.std_logic_unsigned.all;
entity zeyang_xu_wrapper is
    Port( A,B   : in std_logic_vector (3 downto 0);
          decoded_A : out std_logic_vector (6 downto 0);
          decoded_B : out std_logic_vector (6 downto 0);
          decoded_AplusB: out std_logic_vector (13 downto 0));
end zeyang_xu_wrapper;
architecture BehaviorModel of zeyang_xu_wrapper is
    component seven_segment_decoder_zeyang
    port( code           : in std_logic_vector(3 downto 0);
          segments_out : out std_logic_vector(6 downto 0));
    end component;
    component zeyang_xu_bcd_adder
        Port(A: in std_logic_vector(3 downto 0);
              B:           in std_logic_vector(3 downto 0);
              S:           out std_logic_vector(3 downto 0);
              C_out : out std_logic);
    end component;
    (((CODE CONTINUED IN THE NEXT TEXTBOX DUE TO LACK OF SPACE)))

```

```

signal carry: std_logic_vector(3 downto 0);

signal carry_temp: std_logic;
signal result: std_logic_vector(3 downto 0);
signal decode_carry: std_logic_vector(6 downto 0);
signal decode_result: std_logic_vector(6 downto 0);
begin
adder: zeyang_xu_bcd_adder port map (A => A, B=>B, S=>result, C_out=> carry_temp);
carry <= "000"&carry_temp;

decoderA: seven_segment_decoder_zeyang port map(code => A, segments_out => decoded_A);
decoderB: seven_segment_decoder_zeyang port map(code => B, segments_out => decoded_B);

decoder_carry: seven_segment_decoder_zeyang port map(code => carry, segments_out
=>decode_carry);

decoder_result: seven_segment_decoder_zeyang port map(code => result, segments_out
=>decode_result);


decoded_AplusB <= std_logic_vector(unsigned(decode_carry & decode_result));

end BehaviorModel;

```

 Question 2 (2 marks)

Show a representative photo of the board displaying the result of the addition of A and B, where A is the last (right-most) digit of the McGill ID number of one of the students in your group and B is the last (rightmost) digit of the McGill ID number of the other student in the group. Clearly indicate which 7-segment LEDs/ sliding switches are assigned to which inputs/outputs of the circuit on the photo.



A[3-0] is assigned to SW[9-6]

B[3-0] is assigned to SW[5-2]

Decoded_A is assigned to HEX5

Decoded_B is assigned to HEX4

***Decoded_AplusB[13-7] is assigned to
HEX[3]***

***Decoded_AplusB[6-0] is assigned to
HEX[2]***

**N.B: To demonstrate that it can
actually calculate and display
beyond 10, a second photo is also
included showing 8+9 = 17.**

